



TEST PAPER: PHYSICS

Time: 45 Minutes

Class: CBSE 10

Max. Marks: 30 Marks

Date: 12th December 2018


Marking Scheme: All questions carry 10 marks each. Subparts (A) and (B) carry 3 marks each and subpart (C) carries 4 marks.

Question 1:

- Calculate the resistance of 2 km long copper wire of radius 2 mm. (Resistivity of copper = 1.72×10^{-8} in SI units)
- Name the unit of (a) electrical resistance (b) resistivity. Define resistivity.
- State Ohm's law. Write the necessary conditions for its validity. How is this law verified experimentally? What will be the nature of graph between potential difference and current for a conductor? Name the physical quantity that can be obtained from this graph.

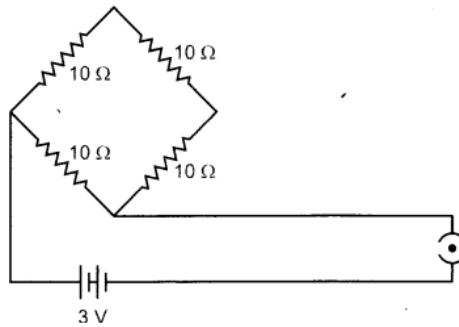
Question 2:

- Find the current drawn from the battery by the network of four resistors Shown in the figure.



- Solve the following:

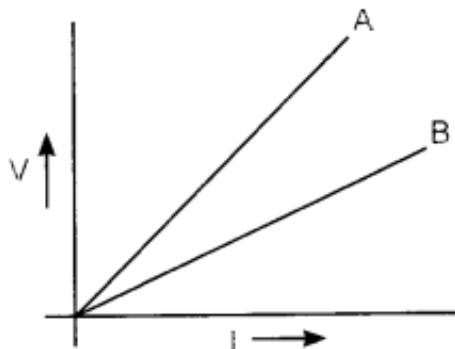- Calculate the amount of work done in carrying a charge of 1 coulomb through a battery of 3 V.
- V-I graph for two wires A and B are shown in the figure. If both wires are of same length and same thickness, which of the two is made of a material of high resistivity? Give justification for your answer.




- Answer the following:

- Define electric power. Express it in terms of potential difference V and resistance R.
- An electrical fuse is rated at 2 A. What is meant by this statement?
- An electric iron of 1 kW is operated at 220 V. Find which of the following fuses that respectively rated at 1 A, 3 A and 5 A can be used in it.

Question 3:

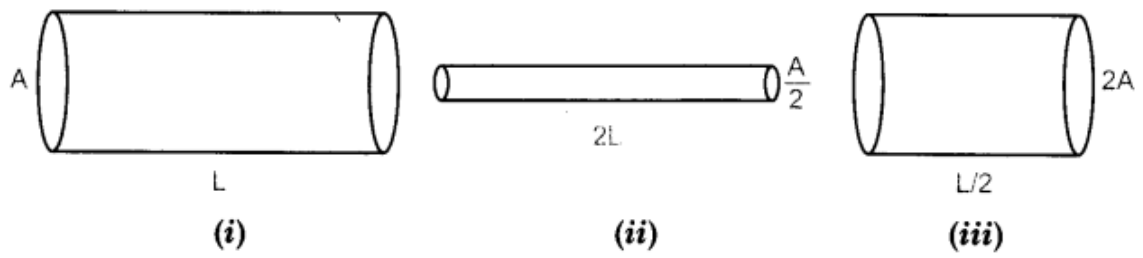- A. The figure below shows three cylindrical copper conductors along with their face areas and lengths. Discuss in which geometrical shape the resistance will be highest.



- B. What is geothermal energy and how do we harness it to generate electricity?
C. Explain the working of a solar cooker with the help of a diagram. State two advantages of using solar cells.